

Introduction to VHDL programming

Juan Antonio Clemente

Translation to the English of the material written by: Marcos Sánchez-Élez
(*Introducción a la programación en VHDL*)

November 13, 2014

Contents

1	Introduction	1
2	Basic Elements of VHDL	3
2.1	Entity	3
2.2	Architecture	4
2.3	VHDL objects	5
2.4	VHDL types	6
2.4.1	Predefined types	6
2.4.2	User-defined types	7
2.4.3	Examples	8
2.4.4	Operators	9
3	Basic Structure of a Source File in VHDL	11
3.1	Concurrent statements	11
3.1.1	WHEN-ELSE	11
3.1.2	WITH-SELECT-WHEN	12
3.2	Conditional statements	13
3.2.1	IF-THEN-ELSE	13
3.2.2	CASE-WHEN	13
3.2.3	FOR-LOOP	14
3.2.4	WHILE-LOOP	14
3.3	<i>Process</i> statement	15
3.4	Structural description	19
3.5	Examples	22
4	Simulation of a VHDL Code	25
4.1	Steps of simulation	25

4.2	Simulation statements	26
4.3	Simulation templates in VHDL	27
5	Description of Sequential Logic	31
5.1	Sequential hardware	31
5.2	Counters	34
5.3	Examples	37
5.3.1	8-bit register	37
5.3.2	8-bit register built using 1-bit flip-flops	37
6	Design of a Finite State Machine (FSM)	39
7	Functions, Procedures and Packages	43
7.1	Functions	43
7.2	Procedures	44
7.3	Examples	44
8	Design of a RAM Memory	47
9	Appendixes	49
9.1	Discussion about using signals vs. variables	49
9.2	Discussion about the effect of incorrectly coding the sensitivity list in a <code>process</code>	50

Chapter 1

Introduction

VHDL is a description language for digital electronic circuits that is used in different levels of abstraction. The VHDL acronym stands for *VHSIC (Very High Speed Integrated Circuits) Hardware Description Language*. This means that VHDL can be used to accelerate the design process.

It is very important to point out that VHDL is NOT a programming language. Therefore, knowing its syntax does not necessarily mean being able to designing digital circuits with it. VHDL is an HDL (Hardware Description Language), which allows describing both asynchronous and synchronous circuits. For this purpose, we shall:

- Think in terms of gates and flip-flops, not in variables or functions.
- Avoid combinatorial loops and conditional clocks.
- Know which part of the circuit is combinatorial and which one is sequential.

Why to use an HDL?

- To discover problems and faults in the design before actually implementing it in hardware.
- The complexity of an electronic system grows exponentially. For this reason, it is very convenient to build a prototype of the circuit previously to its manufacturing process.
- It makes easy for a team of developers to work together.

In particular, VHDL allows not only describing the structure of the circuit (description from more simple subcircuits), but also the specification of the functionality of a circuit using directives, in a similar way as most standard programming languages do.

The most important aim of an HDL is to be able to simulate the logical behavior of a circuit by means of a description language that has many similarities with software description languages.

Digital circuits described in VHDL can be simulated using simulation tools that reproduce the operation of the involved circuit. For this purpose, developers use a set of rules standardized by the IEEE, which explain the syntax of the language, as well as how to simulate it. In addition, there are many tools that transform a VHDL code into a downloadable file that can be used to program a reconfigurable device. This process is named **synthesis**. The way a given tool carries out the synthesis process is very particular, and it greatly differs from what other synthesis tools do.

For XilinxTM users: In this manual we will use the free synthesis tool provided by XilinxTM (Xilinx ISE Web Pack), which can be obtained through the following URL: <http://www.xilinx.com/support/download/index.htm>. All the examples in this manual that may include any coding that is specific from the XilinxTM tool will be highlighted in a box like this one.

TIP: Throughout this manual, boxes like this one will be used to better highlight tips for an efficient programming in VHDL. These tips are a set of basic rules that make the simulation results independent of the programming style. Hence, these rules make the developed code synthesizable, so it can be easily implemented in any platform.

Webs and news related to VHDL programming and its simulation and synthesis tools:

www.edacafe.com: Web page dedicated to spread news related to the world of circuit design. It has a forum of VHDL programming (troubleshooting, free tools ...).

www.eda.org/vasg/: *"Welcome to the VHDL Analysis and Standardization Group (VASG). The purpose of this web site is to enhance the services and communications between members of the VASG and users of VHDL. We've provided a number of resources here to help you research the current and past activities of the VASG and report language bugs, LRM ambiguities, and suggest improvements to VHDL..."*

www.cadence.com: *"Cadence Design Systems is the world's largest supplier of EDA technologies and engineering services. Cadence helps its customers break through their challenges by providing a new generation of electronic design solutions that speed advanced IC and system designs to volume..."*

www.xilinx.com: *"In the world of digital electronic systems, there are three basic kinds of devices: memory, microprocessors, and logic. Memory devices store random information such as the contents of a spreadsheet or database. Microprocessors execute software instructions to perform a wide variety of tasks such as running a word processing program or video game. Logic devices provide specific functions, including device-to-device interfacing, data communication, signal processing, data display, timing and control operations, and almost every other function a system must perform."*

Chapter 2

Basic Elements of VHDL

A digital system is basically described by its inputs and its outputs, as well as how these outputs are obtained from the inputs.

The VHDL code of any circuit is divided into two separate parts: On the one hand, the **entity** specifies the input and output ports of the circuit. On the other hand, the **architecture** describes the behavior of that circuit. An **architecture** must be associated with an **entity**. It is also possible to associate several architectures to the same **entity**, so the programmer can select one of the available ones. This point is explained below in Chapter 2, Section 2.3.

For XilinxTM users: The IEEE library and the following three packets (whose meaning is explained below) appear by default in any source VHDL code created with the XilinxTMISE tool.

```
1  library IEEE;  
   use IEEE.std_logic_1164.all;  
3  use ieee.std_logic_arith.all;  
   use ieee.std_logic_unsigned.all;
```

2.1 Entity


An **entity** is an abstraction of a circuit, either from a complex electronic system or a single logic gate. An **entity** externally describes the I/O interface of the circuit.

The ports of an **entity** can be inputs (**in**), outputs (**out**), input-outputs (**inout**) or **buffer**. The **input** ports can only be read, and they cannot be modified inside the **architecture**. On the other hand, the **output** ports can only be written, but not read. In case an **output** port needs to be read (for instance, to make a decision about its value) or an **input** port needs to be written, they must be instantiated as an **inout** or a **buffer** port. However, in this course we will try to avoid these situations, so the utilization of **inout** and **buffer** ports are beyond the learning outcomes of this course.

The interface described by an **entity** may also include a set of **generic** values that are used to declare properties and constants of the circuits, independently of its **architecture**. **Generics** can have multiple uses: On the one hand, they can be used to define delays in signals and clock cycles (these definitions will not be taken into account at the synthesis level, as explained later throughout this manual). On the other hand, **generics** can also be used as constants that will be used inside the **architecture**. These

constants help to make the code more understandable, portable and maintainable. For instance, the length of a register (in number of bits) can be defined by means of a **generic** parameter. This means that another VHDL code can instantiate this register several times, even if this code instantiates registers with different number of bits. **Generic** parameters are not necessary. Hence, a circuit that does not need them, it simply does not instantiate any **generic** statement in the **entity** declaration.

 The example below shows a description of the **entity** of a circuit. This circuit has two N-bit inputs (A and B) and a single output (Y). Thus, in this case the **entity** description includes a **generic** statement defining a parameter named N whose value is set to 8. This parameter is also used in the declaration of the circuit inputs.



```

1  entity F is
2    generic (N: natural := 8);
3    port (A, B: in bit_vector (N-1 downto 0); Y: out bit);
4  end F;

```

2.2 Architecture

The pairs **entity-architecture** are used in VHDL to completely describe the operation of a circuit. An **architecture** defines how the circuit operates, by including a set of inner signals, functions, procedures, functions... and its description can be either structural or behavioral (details about this will be given in Chapter 3.4).

The code below shows an example of an **architecture**. The association between this **architecture** and the **entity** it refers to is made in the first line (**architecture arch_name of entity_name is**). Next, the code must include the signals, customized types, and components (whose I/O is known) that will be used inside the **architecture**.

```

1  architecture arch_name of entity_name is
2    -- architecture declarations:
3    -- types
4    -- signals
5    -- components
6  begin
7    -- concurrent statements
8    -- conditional statements
9    -- components
10
11    process (sensitivity list) begin
12      -- code
13    end process;
14  end arch_name;

```

The **begin** and the **end** reserved words mark the boundaries of the VHDL code that will actually describe the operation of the circuit. As shown in the example, this code may include: concurrent and

conditional statements, **components** and **processes**. Chapter 3 will get into deeper details about these statements.

It is also possible to define several architectures for the same **entity**. This is better explained in Chapter 9, Section ??.

2.3 VHDL objects

VHDL source codes can include objects. There are three types of objects:

- **Constant:** Objects that have an initial value that is assigned before the simulation. This value shall never be modified during the synthesis or the operation of the circuit. They can be declared before the **begin** of an **architecture**, and/or before the **begin** of a **process**. A constant declaration **MUST** assign a value to it.

```
constant identifier : type := value;
```

- **Variable:** Objects that take a single value that can change during the simulation/execution by means of an assignment statement. Variables are usually used as indexes, mainly in loops, or to take values that allow to model other components. Variables **DO NOT** represent physical connections or memory elements. They can be declared before the **begin** of an **architecture**, and/or before the **begin** of a **process**. A variable declaration **MAY** or **MAY NOT** assign a value to it.

```
1 variable identifier : type [:= value];
```

The assignment of a value to a variable is done by means of the operator **:=**

```
1 name_variable := value;
  i := 10;
```

- **Signal:** Objects that represent memory elements or connections between subcircuits. Contrarily to constants and variables, signals can be synthesized. In other words, a signal in a VHDL source code can be physically translated into a memory element (flip-flop, register...) in the final circuit. They must be declared before the **begin** of the **architecture**. The ports of an **entity** are implicitly declared as signals upon declaration, since they represent physical connections in the circuit.

```
signal identifier : type;
```

The assignment of a value to a signal is done by means of the operator **<=**

```
1 name_signal <= value;
  A <= 10;
```

TIP: If the developed VHDL code only uses constant and signal objects, it will not show any malign effect in the operation of the circuit (see Chapter 9, Sections 9.1 and 9.2). In addition, the obtained code will be easily portable to any other tool. For this reason, unless otherwise stated, all the objects referenced in this manual will be signals.

2.4 VHDL types

In the previous definitions, as well as in the definition of the `entity` ports, it is necessary to define the type of the object. VHDL allows to use predefined types, as well as other user-defined ones.

2.4.1 Predefined types

The most commonly used predefined types are the following ones:

- **bit**: It only admits the values 0 and 1. In order to make an assignment between the object and its value, the latter must be written between single quotes ('0' or '1').
- **bit_vector (range)**: The **range**, always written between brackets, indicates the number of bits of the **bit_vector**, which is an array of 0's and 1's. For an n-bit **bit_vector**, its range must be written in the format N-1 **downto** 0. The bit located to the far left is the most significant one (Most Significant Bit, or MSB), whereas the bit located to the far right is the least significant one (Least Significant Bit or LSB). In order to make an assignment between the object and its value, the latter must be written between quotation marks (i.e., "0011").
- **boolean**: It only can take the values **true** or **false**.
- **character**: It can take any ASCII value.
- **string**: Any chain consisting of ASCII characters.
- **integer range**: Any integer number within the **range**, which in this case is not written between brackets. For instance, 0 **to** MAX. The **range** is optional.
- **natural range**: Any natural number within the **range**. The **range** is optional.
- **positive range**: Any positive number within the **range**. The **range** is optional.
- **real range**: Any real number within the **range**. The **range** is optional.
- **std_logic**: Type predefined in the IEEE 1164 standard. This type represents a multivalued logic comprising 9 different possible values. The most commonly used ones are: '0', '1', 'Z' (for *high impedance*), 'X' (for *uninitialized*) and 'U' (for *undefined*), among others. In order to make an assignment between the object and its value, the latter must be written between single quotes ('0', '1', 'X', ...).
- **std_logic_vector (range)**: It represents a vector of elements of type **std_logic**. Its assignment and definition rules are the same ones as the **std_logic** ones.

For XilinxTM users: For XilinxTM ISE, all the ports of the **entity** must be of type **std_logic** or **std_logic_vector**. The reason is that these two types allow simulating a circuit realistically. For instance, when a signal is instantiated but never initialized in the VHDL code, it will always take the 'U' (*undefined*) value. In addition, XilinxTM ISE translates **natural** and **integer** signals into **std_logic_vector** with the number of bits needed for its complete representation.

In order to use the type **std_logic**, it is necessary to include the following library:

```
use ieee.std_logic_1164.all;
```

In order to use the pre-defined arithmetic and logic functions:

```
1 use ieee.std_logic_arith.all;
```

For vectors that are represented as unsigned binary:

```
1 use ieee.std_logic_unsigned.all;
```

For vectors that are represented as signed binary:

```
1 use ieee.std_logic_signed.all;
```

For vectors that are represented in 2's complement:

```
1 use ieee.std_logic_signed.all;
```

TIP: It is strongly recommended to always use the `std_logic_vector` type independently of the operations that will be made on the involved objects. They can be used as integers or naturals thanks to the `ieee.std_logic_arith.all` and `ieee.std_logic_unsigned.all` libraries. Defining all the signals in the code as `std_logic` or `std_logic_vector` does not complicate the final VHDL code and helps a lot in its integration with XilinxTMISE.

2.4.2 User-defined types

An enumerated type is a data type that comprises a number of user-defined values. Enumerated types are used mainly for the definition of finite state machines.

```
1 type name is (value1, value2, ...);
```

Assuming that `A` has been defined as an enumerated type, the assignment will be as follows: `A <= valuei`; where `valuei` must be one of the enumerated values in the type definition.

Enumerated types are sorted according to their values. Typically, synthesis tools automatically code the enumerated values in such a way that they can be further synthesized. For that purpose, they usually select an ascending sequence or a coding that minimizes the circuit or that maximizes its operating frequency. It may also be possible to directly type the coding by means of ad-hoc directives.

A composed type is a data type comprised by elements of other data types. Composed types can be either **arrays** and **records**.

- An **array** is a data object that comprises a set of elements of the same type.

```
1 type name is array (range) of type;
```

The assignment of a value on a position of the **array** is done by means of integer numbers (see examples at Subsection 2.4.3).

- A **record** is a data object that comprises a set of elements of different types.

```

1  type name is record
      element1: data_type1;
3      element2: data_type2;
      end record;

```

The assignment of a value on an element from a **record** is done by means of a dot (see examples at Chapter 4, Subsection 4.2.3).

Once defined the composed and/or enumerated data type, any signal in the design can be declared of belonging to this new type and this will be done by using the operator defined for signals <=.

2.4.3 Examples

This subsection presents some examples showing how to define and to assign values to signals and variables.

```

2  -- Two dashes are used to introduce comments in the VHDL code
3  -- Examples of definitions and assignments
4
5  constant DATA_WIDTH: integer := 8;
6  signal CTRL: bit_vector(7 downto 0);
7  variable SIG1, SIG2: integer range 0 to 15;
8
9  type color is (red, yellow, blue);
10 signal BMP: color;
11 BMP <= red;
12
13 type word is array (0 to 15) of std_logic_vector (7 downto 0);
14 signal w: word;
15 -- w(integer/natural) <= vector of bits;
16 w(0) <= "00111110";
17 w(1) <= "00011010";
18 ...
19 w(15) <= "11111110";
20
21 type matrix is array (0 to 15)(7 downto 0) of std_logic;
22 signal m: matrix;
23 m(2)(5) <= '1';
24
25 type set is record
26   word: std_logic_vector (0 to 15);
27   value: integer range -256 to 256;
28 end record;
29 signal data: set;
30 data.value <= 176;

```

2.4.4 Operators

Operators can be used to build a wide variety of expressions that allow to calculate data and/or to assign them to signals or variables.

- +, -, *, /, mod, rem: Arithmetic operations.
- +, -: Sign change.
- &: Concatenation.
- and, or, nand, nor, xor: Logical operations.
- :=: Value assignment to constants and variables.
- <=: Value assignment to signals.

```
2  -- Assignment examples
4  y <= (x and z) or d(0);
   y(1) <= x and not z;
6  y <= x1 & x2; -- y = "x1x2"
   c := 27 + r;
```


Chapter 3

Basic Structure of a Source File in VHDL

As previously pointed out, the VHDL code modeling a digital circuit is composed of two parts: an **entity** and one or several **architectures**. The latter contains the statements describing the behavior of the circuit.

```
architecture circuit of name is
2  — signals
begin
4  — concurrent statements (assignment statements to signals)
    process (sensitivity list) begin
6      — conditional statements (assignment statements to
        variables)
    end process;
8 end architecture circuit;
```

Inside the **architecture**, we can find:

- Types and intermediate signals needed to describe its behavior.
- Assignment statements to signals, as well as other concurrent statements.
- Processes, which may contain conditional and/or assignment statements to variables.

3.1 Concurrent statements

Concurrent statements are a kind of assignment statements to signals whose operation depends on a set of conditions. Two kinds of concurrent statements exist:

3.1.1 WHEN-ELSE

```

1  signal_to_modify <= value_1 when condition_1 else
2                               value_2 when condition_2 else
3                               ...
4                               value_n when condition_n else
                               default_value;

```

This statement modifies the value of a given signal depending on a set of conditions, being the assigned values and the conditions independent among each other. The order in which the conditions are sorted determines their preference with respect to the others. In other words, in the previous definition, if `condition_i` is true, then `value_i` will be assigned to `signal_to_modify`, even if any other `condition_j` is also true ($j > i$).

```

1  — Examples WHEN-ELSE
3
4  C <= "00" when A=B else
5        "01" when A < B else
6        "10";
7
8  C <= "00" when A=B else
9        "01" when D = "00" else
10       "10";
11

```

3.1.2 WITH-SELECT-WHEN

```

1  with signal_condition select
2  signal_to_modify <= value_1 when value_1_signal_condition,
3                               value_2 when value_2_signal_condition,
4                               ...
5                               value_n when value_n_signal_condition,
                               default_value when others;

```

This statement is less general than `when-else` one. It modifies the value of a signal, depending on the values that `signal_condition` may have.

```

2  — Example WITH-SELECT-WHEN
3
4  with input select
5  output <= "00" when "0001",
6            "01" when "0010",
7            "10" when "0100",
8            "11" when others;

```

From the point of view of the hardware, these two statements give as a result pure combinatorial hardware; in other words, logic gates, multiplexers, decoders...

TIP: A good VHDL programmer should be used to use these two kinds of sequential statements, since it will avoid having many problems associated to the `if-then-else` statements inside `processes` (explained in Section 3.3).

3.2 Conditional statements

These statements are assignment statements to variables that may or may not be based on a condition. As previously pointed out, they **MUST** be placed inside a **process**. The following conditional statements exist in VHDL:

3.2.1 IF-THEN-ELSE

```

1  process (sensitivity list)
   begin
3  if condition_1 then
   -- assignments
5  elsif condition_2 then
   -- assignments
7  else
   -- assignments
9  end if;
   end process;
```

```

2  -- Example IF-THEN-ELSE
4  process (control, A, B)
   begin
6  if control = "00" then
   output <= A + B;
8  elsif control = "11" then
   output <= A - B;
10 else
   output <= A;
12 end if;
   end process;
```

It is possible to chain as many **if-then-else** statements as desired, as in software description languages, such as Pascal, C, Java...

TIP: **if-then-else** statements should always have an **else**. In addition, as explained in Section 3.3, it is convenient to assign values to the same signals in each one of the branches of the statement, even if the value of some signals should be a *don't care*.

3.2.2 CASE-WHEN

```

2  process (sensitivity list)
   begin
   case signal_condition is
4  when value_condition_1 => -- assignments
   ...
6  when value_condition_n => -- assignments
   when others => -- assignments
8  end case;
   end process;
```

In this case, assignments may also be **if-then-else** statements. The **when others** clause must appear in the statement, but it is not necessary to write any assignment associated to it.

```

1  -----
2  -- Example CASE-WHEN
3  -----
4
5  process (control, A, B)
6  begin
7      case control is
8          when "00" => result <= A+B;
9          when "11" => result <= A-B;
10         when others => result <= A;
11     end case;
12 end process;
13 -----

```

As in other software programming languages, several types of loops are possible:

3.2.3 FOR-LOOP

```

1  process (sensitivity list)
2  begin
3      for var_loop in range loop
4          -- assignments
5      end loop;
6  end process;

```

The **range** can be defined as **0 to N** or as **N downto 0**.

```

1  -----
2  -- Example FOR-LOOP
3  -----
4
5  process (A)
6  begin
7      for i in 0 to 7 loop
8          B(i+1) <= A(i);
9      end loop;
10 end process;
11 -----

```

3.2.4 WHILE-LOOP

```

1  process (sensitivity list)
2  begin
3      while condition loop
4          -- assignments
5      end loop;
6  end process;

```

```

1  -----
2  -- Example WHILE-LOOP
3  -----
4
5  process (A)

```

```

6  variable i: natural := 0;
   begin
   while i < 7 loop
8    B(i+1) <= A(i);
      i := i+1;
10   end loop;
   end process;
12

```

For XilinxTM users: For loops are supported as long as the index range is static (0 to N or N downto 0, where N is a constant) and the loop body does not contain any wait statement. In general, while loops are not supported.

3.3 Process statement

VHDL presents a particular structure named **process** that defines the limits of a code that will be simulated (or executed) if and only if any of the signals included in its sensitivity list has been modified in a previous simulation step.

A **process** features the following structure:

```

2  process (sensitivity_list)
   — Assignments to variables
   — This is optional and, in general, not recommended
4  begin
   — Conditional statements
6  — Assignments to variables or to signals
   end process;

```

Process statements are VERY used in VHDL programming, since, for software programmers, it is very easy to code the behavior of a hardware circuit as if it was a software program. However, this is an important drawback for beginners, since the software-like description of the behavior of the circuit may not actually synthesize into hardware. For this reason, a number of good coding practices exist, which are directly related with the properties of the **process** statement. One should be VERY aware of them in order to code a hardware circuit that simulates and synthesizes correctly.

Property I



Statements existing inside a **process** only run in the instant 0 of simulation OR if any of the signals of the sensitivity list changes.

Problem: The result of the simulation of the circuit may be unexpected due to the “malign effect” of the sensitivity list.

Solution: The sensitivity list MUST include all the signals that are read inside the **process**.

(signal_written <= signal_read).

Let us explain this point by means of an example (Figures 3.1 and 3.2). In this example, no value is assigned to C until the instant 10 ns, although B changes at 5 ns. This happens because the code inside the **process** is not executed unless A changes (this happens at 10 ns). However, at the hardware level, one would expect C to take the value of A as soon as B changes to 1 (at 5 ns). Thus, following the solution proposed above, the correct code should be as follows:

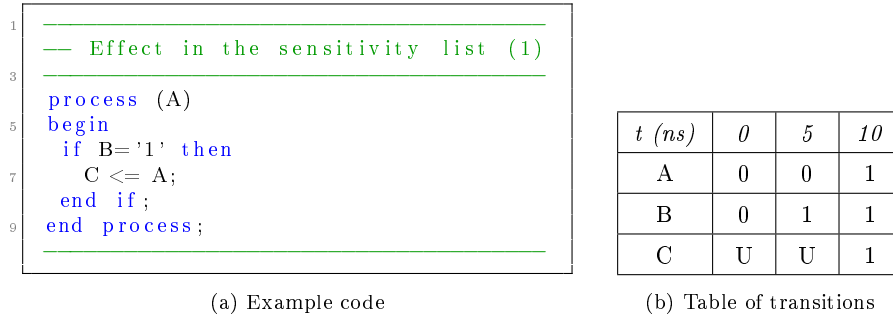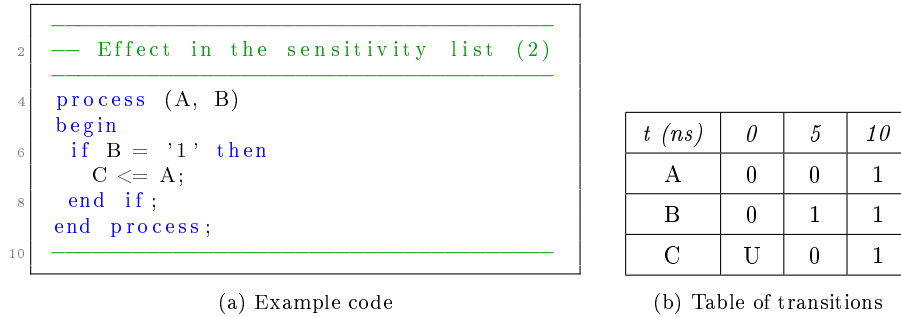Figure 3.1: Example for *Property I* of processes (1)Figure 3.2: Example for *Property I* of processes (2)

Property II



Assignments to signals made inside a **process** have memory.

Problem: If, in a given simulation step, a **process** is executed and as a consequence, a signal **S** is modified; and if in a subsequent simulation step, the **process** is again executed but **S** is not modified inside the code of the **process**, then **C** will conserve the value assigned in the first **process** execution. This may lead to an expected behavior because of the “malign effect” of the **process** memory.

Solution: Conditional statements inside **processes** MUST assign a value to the same set of signals in any of the branches of the statements. In addition, unless it is strictly forbidden at the design level (see Chapter 5), all the conditions MUST have their corresponding **else** branch.

This is explained in the examples of Figures 3.3, 3.4 and 3.5. The first code includes an **else** branch, which means that there is a by-default value for **C** (in this example, at 5 ns). However, the second code does not include this **else** branch. Hence, at 5 ns, both for **Case_1** and **Case_2**, the value of **C** differs in both codes ("00" vs. "10" and "00" vs. "11", respectively). The reason is that processes have memory and in this case, the input combination **A** = "11"; **B** = "10" does not match any branch in the second code. Hence, the value for **C** at 5 ns ("10" for **Case_1** and "11" for **Case_2**) is the same one as in the previous simulation step (i.e., at 0 ns, see the table in Figure 3.4b). In addition, note that, for the code in Figure 3.3a, the output value for **C** is "00" in both **Case_1** and **Case_2** at 5 ns (in both cases, **A** = "11" and **B** = "10"). This is correct; however, this is not true for **Case_2**.

The code in Figure 3.5 is another example of an incomplete conditional statement. In this case, two different values at 5 ns are obtained for **C** and **D** in **Case_3** and **Case_4**, even though the input values are

  Figure 3.3: Example for *Property II* of processes (1)Figure 3.4: Example for *Property II* of processes (2)

exactly the same in both cases ($A = "10"; B = "10"$). This shows us that it is **EXTREMELY** important to make sure that not only the **if-then-else** statement has **else** branch, but also that the very same set of signals are assigned in all the branches. In this case, the problem arises because the **if** branch assigns a value to C, but not to D; whereas the **elsif** assigns a value to D, but not to C.

Property III

All the statements inside a **process** run in parallel, in a similar way as the statements outside a **process** do. However, if inside a **process** a signal is given a value at two different points, the final result will be the one of the last assignment, similarly as what happens in software programming languages. This may turn problematic and not synthesizable if not properly coded.

Solution: It is convenient to double-check that a signal is not assigned twice in the same **process** (this can be done in two different branches of an **if-then-else** statement).

In the following example, at 0 ns and at 10 ns, two values are assigned to C. When the **process** finishes, C takes the last assigned value, the one in the **if** and **elsif** branches, respectively. At 5 ns, C is assigned only one value "00", which is its final value.

```

2  — Conditional incomplete?
4  process (a, b)
5  begin
6      if a = b then
7          c <= a or b;
8      elsif a < b then
9          d <= b;
10     else
11         c <= "00";
12         d <= "11";
13     end if;
14 end process;

```

(a) Example code

Case_3			
t (ns)	0	5	10
A	01	10	11
B	10	10	10
C	UU	10	00
D	10	10	11
Case_4			
A	01	10	11
B	00	10	10
C	00	10	00
D	11	11	11

(b) Table of transitions

Figure 3.5: Example for *Property II* of processes (3)

```

1  — Example of parallel execution
2  — of VHDL statements
5  process (a, b)
6  begin
7      c <= "00";
8      if a = b then
9          c <= a or b;
10     elsif a < b then
11         c <= b;
12     end if;
13 end process;

```

(a) Example code

t (ns)	0	5	10
A	01	11	01
B	10	10	11
C	10	00	11

(b) Table of transitions

Figure 3.6: Example for *Property III* of processes

Property IV

All **process** statements run in parallel.

Problem: In two **processes** P1 and P2 modify the same signal, then it is impossible to know its actual value. (The one assigned by P1 or P2?).

Solution: One should always double-check that a signal is not modified in two or more different processes. In that case, a possible solution is to merge the involved processes.

Property V

The values of all the signals that are modified inside a **process** are not updated until the whole **process** finishes.

Problem: If the sensitivity list is not correctly coded, the update of a signal may be postponed one

or several simulation events. This can be observed in the example of Figure 3.7, where only A is included in the sensitivity list. The example in Figure 3.8 does not present this problem any more.

Solution: As in *Property IV*, always double-check that a signal is not modified in two or more different processes.

```

2  — Wrong sensitivity list
4  process (A)
5  begin
6    B <= A;
7    C <= B;
8  end process;

```

(a) Example code

t (ns)	0	5	10
A	0	1	0
B	0	1	0
C	U	0	1

(b) Table of transitions

Figure 3.7: Example for *Property V* of processes (1)

```

2  — Sensitivity list OK
4  process (A, C)
5  begin
6    C <= A;
7    B <= C;
8  end process;

```

(a) Example code

t (ns)	0	5	10
A	0	1	0
B	0	1	0
C	0	1	0

(b) Table of transitions

Figure 3.8: Example for *Property V* of processes (2)

3.4 Structural description

This description is used to create an **architecture** that instantiates other entities that have already been defined elsewhere. This makes possible to build hierarchical descriptions of circuits, which improves their reusability and scalability.

In order to do this, such an **architecture** must declare the entities that will be instantiated as components, and add as many instances of these components as needed in the body of the **architecture**, as the following code illustrates. Structural descriptions are very useful in bottom-up hierarchical designs.

```

architecture circuit of name is
2  component subcircuit
3    port (...);
4  end component;

6  — signals
7  ...
8  begin
9    — "chip_i" is the name of the instance declared in this code
10   — "subcircuit" is the name of the component that is used
    chip_i: subcircuit port map (...);

```

```

12 | — This can be combined with behavioral descriptions
    | end circuit;

```

The **architecture** may add as many instances of the same **component** as needed. The only restriction that VHDL imposes is that each one of the **component** instances must be given a different name in the body of the **architecture**.

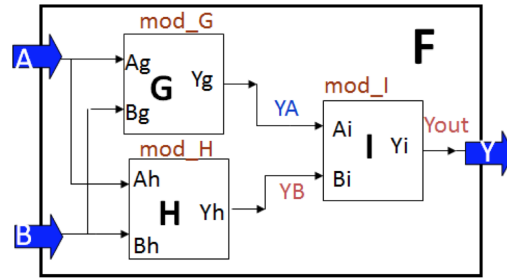


Figure 3.9: Example of a structural description of an **entity**

The code below is an example of a structural description of the circuit depicted in Figure 3.9. Note that, in order to make the interconnections needed between the output of a **component** and the input of another one, intermediate signals are needed.

```

1  — Example structural description
3
5  library IEEE;
6  use IEEE.std_logic_1164.all;
7  use ieee.std_logic_arith.all;
8  use ieee.std_logic_unsigned.all;
9
10 entity F is
11     port (A, B: in std_logic; Y: out std_logic);
12 end F;
13
14 architecture structural of F is
15
16     component G
17         port (Ag, Bg: in std_logic; Yg: out std_logic);
18     end component;
19     component H
20         port (Ah, Bh: in std_logic; Yh: out std_logic);
21     end component;
22     component I
23         port (Ai, Bi: in std_logic; Yi: out std_logic);
24     end component;
25     signal YA, YB, Yout: std_logic;
26
27 begin
28     mod_G: G port map (A, B, YA);
29     mod_H: H port map (A, B, YB);
30     mod_I: I port map (YA, YB, Yi);
31     Y <= Yi;
32 end structural;

```


IMPORTANT: In this example, note that the Y intermediate signals are needed, whereas no intermediate signal is needed in order to connect the inputs of the **entity** F (A and B) and the inputs of components **mod_G** and **mod_H**.

Structural descriptions of circuits can also be made by means of **generate** statements. These statements are used to automatically create an array of instances of the same **component** and/or other concurrent statements. The syntax of the **generate** statement is as follows:

```

1  for index in range generate
2  — range can be 0 to N or N downto 0; N being a constant
3  — concurrent statements
4  — component instances
5  end generate;
```

The two following examples show how **generate** instances are instantiated and used in a VHDL code:

```

1  — Example GENERATE 1
2
3  signal a, b: std_logic_vector(0 to 7)
4  ...
5  gen1: for i in 0 to 7 generate
6      a(i) <= not b(i);
7  end generate gen1;
```

```

1  — Example GENERATE 2
2
3  component subcircuit
4  port( x: in std_logic; y: out std_logic);
5  end component comp
6  ...
7  signal a, b: std_logic_vector(0 to 7);
8  ...
9  gen2: for i in 0 to 7 generate
10     u: subcircuit port map(a(i), b(i));
11 end generate gen2;
```

Component instantiations in **generate** statements can also include conditions, as long as they are referred to the index of the **for** in the **generate** statement. The following code shows an example of this:

```

1  — Example GENERATE 3
2
3  signal a, b: std_logic_vector(0 to 7)
4  ...
5  loop_1: for i in 0 to 7 generate
6      condition: if i > 0 generate
7          a(i) <= b(i-1);
8      end generate condition;
9  end generate loop_1;
```

This example assigns the values of the vector **b** to the vector **a**, by left-shifting them 1 position. However, it does not assign any value to **a(0)**, since in that case, the condition in the **generate** statement is not met.

However, the following code (which is NOT correct), the generated hardware depends on the value of **b(i)**, which is not known at design time. Since the actual value of the **b** vector depends on the execution of the circuit at any point of time, it is not possible to generate any hardware with this **generate** statement.

```

1  -----
2  -- Example GENERATE 4
3  -----
4  signal a, b: std_logic_vector(0 to 7)
5  ...
6  loop_1: for i in 0 to 7 generate
7      condition: if b(i) = '0' generate
8          a(i) <= b(i-1);
9      end generate condition;
10     end generate bucle;
11  -----

```

3.5 Examples

2:1 multiplexer

A possible **entity** description for this module would be as follows:

```

1  -----
2  -- Entity declaration for a 2:1 MUX
3  -----
4  entity mux2 is
5      port (D0, D1, S0: in std_logic; O out std_logic);
6  end mux2;
7  -----

```

Table 3.1: Truth table of a 2:1 multiplexer

S0	O
0	D0
1	D1

Table 3.1 summarizes the operation of a 2:1 multiplexer, which can be coded in VHDL as follows:

```

1  -----
2  -- Behavioral VHDL code for a 2:1 MUX (1)
3  -----
4  architecture behavioral_1 of mux2 is
5      begin
6          O <= D1 when (S0 = '1') else D0;
7      end behavioral_1;
8  -----

```

or as follows:

```

2  — Behavioral VHDL code for a 2:1 MUX (2)
4  architecture behavioral_2 of mux2 is
5  begin
6      multiplexer: process(D0,D1,S0)
7          if (S0 = '1') then
8              O <= D1;
9          else
10             O <= D0;
11         end if;
12     end process;
13 end behavioral_2;
14

```

However, we also know that the operation of this circuit is equivalent to the truth table of the circuit depicted in Figure 3.10.

 


Figure 3.10: Structural description of a multiplexer

Which is equivalent to the following structural code:

```

2  — Structural VHDL code for a 2:1 MUX
4  architecture structural of mux2 is
5  begin
6      — component declarations
7      component AND2
8          port (I0,I1: in std_logic; O: out std_logic);
9      end component;
10     component OR2
11         port (I0,I1: in std_logic; O: out std_logic);
12     end component;
13     component INV
14         port (I0,I1: in std_logic; O: out std_logic);
15     end component;
16
17     — signal declarations
18     signal S1,S2,S3: std_logic;
19
20     begin
21         U1: INV port map (S0,S1);
22         U2: AND2 port map (D0,S1,S2);
23         U3: AND2 port map (S0,D1,S3);
24         U4: OR2 port map (S2,S3,O);
25     end structural;
26

```

Or the following behavioral code:

```
2  — Hybrid structural/behavioral VHDL code for a 2:1 MUX
4  architecture mixed of mux2 is
5      signal S1,S2: std_logic;
6  begin
7      S1 <= D0 and not S0;
8      S2 <= D1 and S0;
9      O <= S1 or S2;
10 end mixed;
```

Chapter 4

Simulation of a VHDL Code

Typically, simulation tools used for VHDL programming follow a discrete event time model for simulating circuits described in this language. This means that these simulators model the operation of a system as a discrete sequence of events in time. Events occur each time any signal changes its value. This marks a potential change of state in the circuit. Between two consecutive events, no change in the system is assumed to occur. Thus, the simulation can directly jump in time from one event to the next one, independently of the time elapsed between them (i.e., just a few picoseconds or several seconds).

4.1 Steps of simulation

VHDL simulations comprise three steps:

- **Step 0:** All the signals are initialized and the time count is set to 0.
- **Step 1:** All the transitions scheduled for that time are carried out.
- **Step 2:** All the signals that are modified as a consequence of transitions occurring at instant t are written down in the list of events and scheduled for instant $t + \delta$, where δ is infinitesimal.

Steps 1 and 2 are repeated as many times as necessary until no more transitions exist. As previously stated, the values assigned to signals remain constant from one event to the following one.

The examples in Figures 4.1, 4.2 and 4.3 illustrate these three simulation steps. On the one hand, Examples 1 and 2 simulate two concurrent assignments that are placed outside a **process**, where **A** takes value '0' at 0 ns, and '1' at 5 ns.

```
1 B <= A;
  C <= B;
```

(a) Example code

t (ns)	0	$0+\delta$	No more changes	5	$5+\delta$	No more changes
A	0	0		1	1	
B	U	0		0	1	
C	U	0		0	1	

(b) Table of transitions

Figure 4.1: Example 1: Simulation steps in VHDL

2	<div style="border: 1px solid black; padding: 5px; display: inline-block;"> C <= B; B <= A; </div>	$t \text{ (ns)}$	0	$0+\delta$	$0+2\delta$	No more changes	5	$5+\delta$	$5+2\delta$	No more changes
		A	0	0	0		1	1	1	
		B	U	0	0		0	1	1	
		C	U	U	0		0	0	1	

(a) Example code

(b) Table of transitions

Figure 4.2: Example 2: Simulation steps in VHDL

On the other hand, in the following example, the two assignments are made inside a **process** with a sensitivity list:

2	4	<div style="border: 1px solid black; padding: 5px; display: inline-block;"> <pre>process (A) begin B <= A; C <= B; end process;</pre> </div>	$t \text{ (ns)}$	0	$0+\delta$	No more changes	5	$5+\delta$	No more changes
			A	0	0		1	1	
			B	U	0		0	1	
			C	U	U		U	0	

(a) Example code

(b) Table of transitions

Figure 4.3: Example 3: Simulation steps in VHDL

In this case, we can observe that the output value at the end of the simulation in Figure 4.3b differs from what was obtained in Figures 4.1b and 4.2b ($B='1'$ and $C='0'$). Let us analyze in detail what is happening in this example: At 0 ns, the **process** is executed, B is assigned the value of A, and C is assigned the value that B had before the **process** execution (which is 'U' or "undefined"). At $0+\delta$, A does not change, hence the **process** is not executed again and all the signals keep their values. The simulation is resumed at 5 ns, when A changes (from '0' to '1'). Hence, the **process** is executed again and as a consequence, B is assigned the value of A, and C is assigned the value that B had before this new **process** execution (which is '0'). In this new simulation step ($5+\delta$), A does not change, hence the **process** is not executed again and the signal values do not change. Figures 4.4 and 4.5 show what could be seen in any VHDL simulator. Note that δ is infinitesimal and therefore, not visible in the simulation.



Figure 4.4: Simulation results for Examples 1 and 2

Obviously, the simulation result obtained in the table of Figure 4.5 is incorrect. This can be easily solved by adding B to the sensitivity list of the **process**.

4.2 Simulation statements

VHDL features the **wait** statement, which stops the simulation of the code until a condition is met. A **process** must include a **wait** statement if it does not have any sensitivity list. In addition, it is also

 


Figure 4.5: Simulation results for Example 3

possible to generate sequential hardware by using `wait` statements. Chapter 5 makes a deeper discussion about this. There are three types of `wait` statements:

- `wait on list_of_signals;` The simulation stops until any signal in the `list_of_signals` is modified.
- `wait for time;` The simulation stops for the time specified in the `time` variable.
- `wait until condition;` The simulation stops until the `condition` is met.

The following code illustrates the operation of the `wait` statement. In this example, `C` cannot be updated unless `A` is '1', which occurs at 5 ns.

```

1  process
2  begin
3      B <= A;
4      wait until A = '1';
5      C <= B;
6  end process

```

(a) Example code

t (ns)	0	$0+\delta$	No more changes	5	$5+\delta$	$5+2\delta$	No more changes
A	0	0		1	1	1	
B	U	0		0	1	1	
C	U	U		0	0	1	

(b) Table of transitions

Figure 4.6: Example: Operation of the `wait` statement

4.3 Simulation templates in VHDL

Many simulation and synthesis tools include a graphical user interface (GUI) to help to set the stimuli to the circuit inputs in order to check if the design works correctly. However, for large circuits and/or large test benches, it is much more practical to create a testbench directly using VHDL.

 


Figure 4.7: RTL description of a simulation template for testbenches in VHDL

Either if the testbench has been created by using the GUI or it has directly typed, the final result will be a VHDL file containing an `entity` without any inputs or outputs, and that instantiates two `process` and a `component`, as indicated in Figure 4.7. The latter actually instantiates the circuit under test.

It is important to know what a VHDL testbench file looks like. First of all, it must include the following libraries:

```

2  — Libraries to be added in a VHDL testbench
4  library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
6  use IEEE.STD_LOGIC_ARITH.ALL;
7  use IEEE.STD_LOGIC_UNSIGNED.ALL;
8  use IEEE.STD_LOGIC_TEXTIO.ALL;
9  use STD.TEXTIO.ALL;
10

```

Next, an **entity** without any inputs or outputs must be created:

```

2  entity simulation is
3  end simulation;

```

Next, the **architecture** is described, which includes the processes and the components of the circuit under test (if any), as described above. A possible template to instantiate the circuit under test and the **process** to set stimuli to its input signals could be as follows:

```

2  — Template for VHDL testbench architecture
4  architecture testbench_arch of simulation is
6      component circuit
7      port (input: in std_logic; ...; output: out std_logic);
8      end component;
10     — Intermediate signals, with the same name and type than
11     — those of the circuit under test
12     signal input: std_logic := '0';
13     ...
14     signal output: std_logic;
15     — Output signals are not initialized
16
17 begin
18
19     UUT : circuit port map (input, ..., output);
20
21     process
22     begin
23         wait for 200 ns;
24         input <= '1';
25         ...
26
27         wait for 100 ns; — Total: 300 ns
28         input <= '0';
29         ...
30
31         wait for T ns; — Total: 300 + T ns
32         input <= '1';
33         ...
34
35         wait for ...
36         ...

```



```

38     wait for 100 ns;
    end process;
40 end testbench_arch;

```

The first `wait` of the code (`wait for 200 ns;`) keeps the input signal to its initial value ('0') for the first 200 ns. Then, the following statements are executed, among which the assignment `input <= '1'`. The second `wait` (`wait for 100 ns;`) keeps this new value for another 100 ns.

The following code is another example, which simulation result is depicted in Figure 4.8.

```

1  — Example for the input stimuli process in a VHDL testbench
2
3  process
4  begin
5      wait for 5 ns;
6      A <= '1';
7
8
9      wait for 5 ns;    — Total: 10 ns
10     A <= '0';
11
12
13     wait for 10 ns;   — Total: 20 ns
14     A <= '1';
15
16
17     wait for 5 ns;    — Total: 25 ns
18     A <= '0';
19
20     wait for 10 ns;
21 end process;

```

 


Figure 4.8: Example of a signal simulation, whose values are set manually

The second `process` included in the VHDL template defines the clock signal very easily:

```

2  — Template for the process that defines the clock
3
4  process
5  begin
6      wait for 10 ns;
7      CLOCK_LOOP : loop
8          clk <= '0';
9          wait for time_low ns;
10         clk <= '1';
11         wait for time_high ns;
12     end loop CLOCK_LOOP;
13 end process;
14

```

Through the `loop` statement, this `process` generates a signal (`clk`) whose value is set to '0' and to '1' alternatively, according to the times specified in the `time_low` and `time_high` constants. The first

`wait` statement keeps the initial value of `clk` for the first 10 ns. Then, the second `wait` indicates the time that `clk` is set to its low value ('0'). Finally, the last `wait` indicates the time that `clk` is set to its high value ('1'). This sequence is repeated forever. Note that this is possible thanks to the `loop` statement. Actually, this is a slight variation with respect to the `for-loop` and `while-loop` ones statements, already described in Chapter 3, Section 3.2. In this case, since the `loop` statement does not have any condition, it never stops iterating. In other words, it will iterate until the final execution of the testbench.

Chapter 5

Description of Sequential Logic

As previously explained in Chapter 3, Section 3.3, one of the most important properties of processes is their ability to keep the values assigned to signals inside them, as long as the **process** is not executed again or a subsequent execution of that **process** does not assign any other value to that signal (see *Property II* in Chapter 3, Section 3.3). For this reason, processes can be used to describe sequential logic.

IMPORTANT: Processes being used to describe sequential logic DOES NOT mean that the statements comprised in that **process** run sequentially.

5.1 Sequential hardware

Processes can be used in order to describe flip-flops and registers. To this end, the **'event** attribute can be used on the clock signal as follows:

```
if (clk 'event and clk = '1') then ...
```

The **'event** attribute on a signal returns true if that signal has just been modified, and it returns false otherwise. The previous **if-then** statement checks if there has been any modification on the **clk** signal, and if its new value is '1'. Thus, it recognizes a rising edge in the clock signal. Using this concept, a D flip-flop can be described as follows:

```
1  — D Flip-Flop
3
4  entity D_FF is
5      port (d, clk: in bit; q: out bit);
6  end D_FF;
7  architecture ARCH of D_FF is
8  begin
9      process (clk, d)
10     begin
11         if (clk 'event and clk = '1') then q <= d; end if;
12     end process;
13 end ARCH;
```

However, typically a D flip-flop has also a reset signal. In case this signal was asynchronous, it could be implemented as follows:

```

2  -- D Flip-Flop with asynchronous reset
4  entity D_FF_SReset is
5      port(d, clk, reset: in bit; q: out bit);
6  end D_FF_SReset;
8  architecture ARCH_ASYN of D_FF_SReset is
9  begin
10     process (clk, reset, d)
11     begin
12         if (reset = '1') then q <= '0';
13         elsif clk = '1' and clk'event then q <= d;
14         end if;
15     end process;
16 end ARCH_ASYN;

```

As this code shows, the **process** runs if there is any change in the **clk**, **reset** or **d** signals, as indicated in its sensitivity list. Then, the **if-then** statement checks if the **reset** signal has been set to '1'. In that case, the output value of the FF is set to '0'. Otherwise, the **clk** signal is checked in a similar way as in the D flip-flop example.

Finally, a possible code for a D flip-flop with synchronous **reset** could be as follows:

```

1  -- D Flip-Flop with synchronous reset
3  architecture ARCH_SYN of D_FF_ASReset is
4  begin
5      process (clk, reset, d)
6      begin
7          if clk = '1' and clk'event then
8              q <= d;
9              if (reset = '1') then q <= '0';
10             end if;
11         end if;
12     end process;
13 end ARCH_SYN;
15

```

For XilinxTM users: In general, in order to create sequential hardware with the expected behavior, the following rules must be fulfilled:

- An **if-then** statement used to detect a clock edge cannot have an **else** branch. Otherwise, the **else** branch would always run, except the precise moments when the clock signal changes.
- In **if-then-elsif** statements, the edge in a clock signal can only be detected in the last branch of the **if-then-elsif** sentence (which **MUST NOT** have an **else** branch).
- An **if-then** statement used to detect a clock edge can have as many chained **if-else** statements as necessary.
- A **process** can only have one edge detection. Otherwise, it would mean that the specified hardware would be sensible to several clock signals. This is far beyond the objectives of this course.

These ideas are illustrated by means of the examples depicted in Figures 5.1, 5.2 and 5.3. The difference between the codes in Figures 5.1a and 5.2a is the order in the assignment of values to **a**, **b** and **c**. In Figure 5.1a, this assignment would be done as in any other software description language. However, in Figure 5.2a, one could think that the assignments are incorrect. In order to understand the results, one should remember Properties IV and V, already described in Chapter 3, Section 3.3:

*Property IV: All **process** statements run in parallel. Hence, the order in which the assignments appear in the code is not relevant to the final result.* This explains why, for Figures 5.1b and 5.2b, the values of the outputs **b** and **c** are the same ('1' and '0' at 5 ns; '1' and '1' at 10 ns) in both cases.

*Property V: The values of all the signals that are modified inside a **process** are not updated until the whole **process** finishes.* This explains why the value of **c** is not updated at 5 ns, but at 10 ns.

```

1  -----
2  -- Example 1
3  -----
4  process (clk, a, b, reset)
5  begin
6      if reset = '1' then
7          b <= '0';
8          c <= '0';
9      elsif clk'event and clk = '1' then
10         b <= a;
11         c <= b;
12     end if;
13 end process;

```

(a) Example code

clk edge	0 ns	5 ns	10 ns
reset	1	0	0
a	1	1	1
b	0	1	1
c	0	0	1

(b) Table of transitions

Figure 5.1: Example 1: Sequential hardware description

Finally, in the code of Figure 5.3a, **b** and **c** are directly assigned the value of **a**. As a consequence, both signals are updated simultaneously.

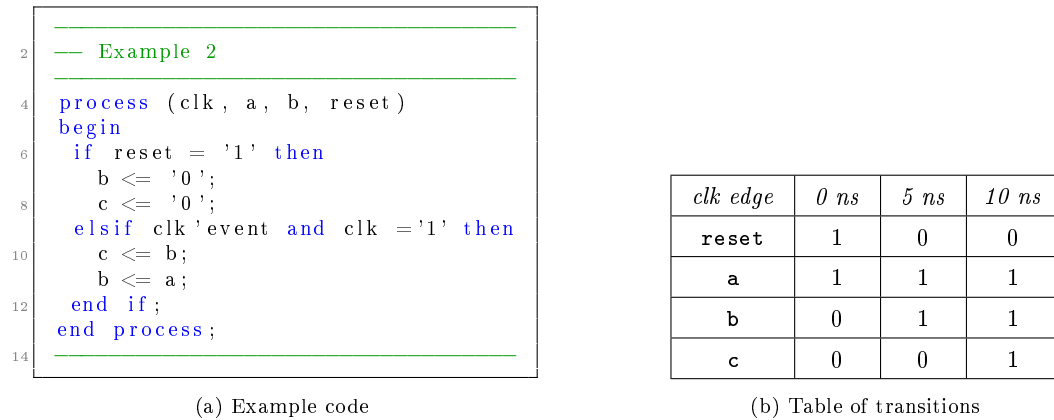


Figure 5.2: Example 2: Sequential hardware description

 


Figure 5.3: Example 3: Sequential hardware description

5.2 Counters

One of the most common components of digital circuits are counters. A “possible” way of describing a counter would be by means of the following code. However, it does not work as a counter. **WHY?**

```


2  -- Counter: Wrong code
4  entity contador is
5      port (reset : in std_logic; n : out std_logic_vector(3 downto 0));
6  end contador;
8
9  architecture arch of contador is
10     signal intermediate: std_logic_vector(3 downto 0);
11 begin
12
13     process (reset, intermediate)
14     begin

```

```

14   if (reset = '1') then
15       intermediate <= "000";
16   else
17       intermediate <= intermediate + 1;
18   end if;
19 end process;
20 n <= intermediate;
21
22 end arch;

```

 

(a) Scheme for a feedback counter

t (ns)	0	$0+\delta$	No more changes	5	$5+\delta$	$5+2\delta$	$5+3\delta$	$5+4\delta$...
reset	0	0		0	0	0	0	0	0
intermediate	U	0		0000	0001	0010	0011	0100	...

(b) Table of transitions

Figure 5.4: Example of a badly coded counter

The reason is simple: The code above does not manage the update of the output signal in a controlled way (i.e., following a clock signal). This means that the inferred circuit from that code would look like as in Figure 5.4a. This is not a sequential circuit, but a combinatorial one, which implementation makes no sense whatsoever. A behavioral simulation of this circuit would not make any sense either. This is illustrated in Figure 5.4b, where the counter never stops iterating after its input has been set to '1' (in this example, this is assumed to happen at 5 ns).

As we already know, a counter is a sequential circuit that is controlled by means of a clock signal. This makes possible to generate an ascending or descending sequence whose values are generated each new clock cycle. Therefore, a VHDL code for a counter must include clock edge recognition (for instance, with the 'event attribute).

```

1  — Example of a mod-8 counter
3
5  entity counter is
6      port (reset, clk: in std_logic; n: out std_logic_vector(3 downto 0));
7  end counter;
8
9  architecture arch of counter is
10     signal intermediate: std_logic_vector(3 downto 0);
11 begin
12     process (reset, clk, intermediate)
13     begin
14         if (reset = '1') then

```

```

15     intermediate <= "000";
16     elsif clk'event and clk = '1' then
17         intermediate <= intermediate + 1;
18     end if;
19 end process;
20 n <= intermediate;
21
22 end arch;
23

```

The signal `intermediate` is defined as a `std_logic_vector(3 downto 0)`. By applying the rules of the IEEE standard, we have `"1111" + '1' = "0000"`. Thus, the code above implements an ascending count that follows the sequence `[0..15]` and then, it starts over again.

For XilinxTM users: XilinxTM tools need VHDL descriptions of circuits to include a `reset` signal. It can be either asynchronous (as in the previous example) or synchronous. This makes possible to design counters that are updated until they reach a given maximum value and then they are initialized to 0; or counters that stay in that maximum value; or counters that start from a given value that can be previously loaded using a `load` signal. All these functionalities can be described by using `if-then-else` statements inside the `elsif clk'event and clk = '1' then...` branch.

Thus, the following example describes a generic counter that, once it reaches a maximum value, is re-initialized and starts over again.

```

1  -- Example of a counter that is re-initialized after reaching a maximum value
2  --
3
4  entity counter is
5      generic (maximum: natural := max; N: natural := 8);
6      port (reset, clk : in std_logic; n: out std_logic_vector(N-1 downto 0));
7  end counter;
8
9  architecture arch of counter is
10     signal intermediate: std_logic_vector(N-1 downto 0);
11 begin
12
13     process (reset, clk, intermediate)
14     begin
15         if (reset = '1')
16             intermediate <= "000";
17         elsif clk'event and clk = '1' then
18             if intermediate < max
19                 intermediate <= intermediate + 1;
20             else
21                 -- This statement sets all the bits in "intermediate" to 0
22                 intermediate <= (others=>'0');
23             end if;
24         end if;
25     end process;
26
27     n <= intermediate;
28
29 end arch;

```


5.3 Examples

5.3.1 8-bit register

```

2  — 8-bit register: behavioral description
4  entity register_8 is
5    port (clk, reset: in bit;
6          A: in bit_vector(7 downto 0);
7          B: out bit_vector(7 downto 0));
8  end register_8;
10 architecture behavioral of register_8 is
11 begin
12   process(clk, reset)
13   begin
14     if reset = '1' then B <= "00000000";
15     elsif (clk'event and clk='1') then B <= A;
16     end if;
17   end process;
18 end behavioral;

```

5.3.2 8-bit register built using 1-bit flip-flops

```

1  — 8-bit register: structural description
3  entity FF is
4    port (clk, reset, C: in bit; D: out bit);
5  end FF;
7  architecture arch of FF is
8  begin
9    process(clk, reset)
10   begin
11     if reset = '1' then D <= '0';
12     elsif (clk'event and clk='1') then D <= C;
13     end if;
14   end process;
15 end arch;
17 entity register_8 is
18   port (clk, reset: in bit;
19         A: in bit_vector(7 downto 0);
20         B: out bit_vector(7 downto 0));
21 end register_8;
23 architecture structural of register_8 is
24   component FF
25     port (clk, reset, c: in bit; d: out bit);
26   end component FF;
27   signal F: bit_vector(7 downto 0);

```

```
31 begin
   gen: for i in 0 to 7 generate
33     u: FF port map(clk, reset, A(i), F(i));
       end generate gen;
35     B <= F;
   end structural;
37
```

Chapter 6

Design of a Finite State Machine (FSM)

VHDL allows to describe finite state machines (FSMs) at the algorithmic level. This makes possible to easily coding the operation of any FSM without having to actually write the state transition and the output functions.

The register transfer level description of a FSM looks like as indicated in Figure 6.1. There are many ways of describing FSMs in VHDL. The one proposed in this chapter is valid to any synthesis tool that works with this programming language.

 


Figure 6.1: RTL description of a finite state machine (FSM)

First of all, one must define an enumerated type including all the identifiers of the states. It is practical to select representative names for the states. The synthesis tool will be able to assign a binary code to each one of them.

```
1 type STATES is (up, down, stop, ...);
```

Next, the body of the **architecture** must define the state transition function (F) and the output function (G); as well as the ability to change from one state to the following one. For this purpose, two processes are defined:

- The first one codes F and G functions. In other words, depending on the current state, it specifies the new values of the state and the output(s).
- The second one is a sequential **process** that models the flip-flops for the state. Hence, its only objective is to update the current state of the FSM.

Let us illustrate this in greater detail by means of an example. Let a FSM be a sequence recognizer that detects the sequence "001" that comes through a serial input E. It is assumed that E is synchronized with a clock signal. This sequence recognizer can be implemented as the Moore machine depicted in Figure 6.2 with the following four states:

- S1: Wait for the first '0' in the sequence.
- S2: Wait for the second '0' in the sequence.
- S3: Wait for the '1' in the sequence.
- S4: Activate the output signal.

 


Figure 6.2: Example Moore machine for a FSM

Thus, for the VHDL implementation, the first step is to define an enumerated type that comprises the 4 states involved:

```

1  type STATES is (S1, S2, S3, S4);
   signal STATE, NEXT_STATE: STATES;

```

Next, a couple of processes must determine the value of the next state (NEXT_STATE) and the output (O), depending on the value of current state (STATE) and the input (E). This is illustrated by means of the code below. On the one hand, the **SYNCHRONOUS process** implements the transition of the FSM from its current state to its next state each clock cycle. On the other hand, the **COMBINATORIAL process** defines both the next state depending on the current state and the value of the FSM input E, as well as the value of the output O, which in this case, only depends on the current state.

```

library IEEE;
2  use IEEE.std_logic_1164.all;

4  entity FSM is
    port(reset, E, clk: in bit; O:
        out bit);
6  end FSM;

8  architecture ARCH of FSM is
    type STATES is (S1, S2, S3, S4);
    signal STATE, NEXT_STATE: STATES;
    begin

12     SYNCHRONOUS: process(clk, reset)
14     begin
        if reset = '1' then
16         STATE <= S1;

```

```

    elsif clk'event and clk='1'
    then
18      STATE <= NEXT_STATE;
    end if;
20 end process SYNCHRONOUS;

22 COMBINATORIAL: process(STATE,E)
begin
24   case STATE is
    when S1 =>
26     O <= '0';
        if (E='0') then
28         NEXT_STATE <= S2;
        else
30         NEXT_STATE <= S1;
        end if;
32   when S2 =>
        O <= '0';
34     if (E='0') then
        NEXT_STATE <= S3;
36     else
        NEXT_STATE <= S1;
38     end if;
    when S3 =>
40     O <= '0';
        if (E='0') then
42         NEXT_STATE <= S3;
        else
44         NEXT_STATE <= S4;
        end if;
46   when S4 =>
        O <= '1';
48     if (E='0') then
        NEXT_STATE <= S2;
50     else
        NEXT_STATE <= S1;
52     end if;
    end case;
54 end process COMBINATORIAL;
end ARCH;

```

For XilinxTM users: XilinxTM might not be able to recognize a FSM. In this case, it may delete many intermediate signals and group conditions. If we want XilinxTM to recognize the FSM, the following two rules must be fulfilled:

- The state machine must include a reset so it can be initialized.
- The combinatorial **process** must ALWAYS assign a value to NEXT_STATE (even if this may seem redundant).

Chapter 7

Functions, Procedures and Packages

VHDL supports two kinds of subprograms (**functions** and **procedures**) that greatly help to improve the description, scalability and reusability of the code. A number of these subprograms can be gathered under a common structure named **package**, as shown in the code below:

```
1 package p is
2     function fname (input_signals) return type;
3     procedure pname (input_signals; output_signals);
4 end p;
5
6 package body p is
7     ...
8 end p;
```

7.1 Functions

They are used to carry out punctual calculations and they return a value instantly.

- They cannot modify their input parameters.
- They cannot modify signals or variables externally declared to the function.
- They always return a value whose type has been specified in the function declaration.
- Their execution time is 0. Hence, they cannot contain any **wait** statement.

The syntax of functions is as follows:

```
function identifier (...) return type
— Signals, variables
begin
— Function body
— It can use any VHDL statement
return value;
end function identifier;
```

7.2 Procedures

Procedures constitute another way to describe small circuits.

- They can exchange data bidirectionally with the outside world.
- They can contain `wait` statements.
- They can assign values to signals.
- They are defined in the declarations zone of the `architecture`.

```

1  procedure name(parameters)
   — signals, variables
3  begin
   — body of the procedure
5  end procedure name;
```

7.3 Examples

The package pf the code below includes various functions for converting data from `vector` to `natural` and viceversa, as well as a `procedure` to add vectors.

```

1  library IEEE;
   use IEEE.std_logic_1164.all;

3
   package arith_operations is
5     function vector_to_natural (v:in std_logic_vector) return natural;
     function natural_to_vector (nat : in natural; length : in natural)
7       return std_logic_vector;
     procedure vector_add (v1, v2 : in std_logic_vector; vo : out std_logic_vector);
9   end arith_operations;

11  package body arith_operations is

13     function vector_to_natural (v:in std_logic_vector) return natural is
       variable aux : natural:=0;
15     begin
       for i in v'range loop
17         if v(i)='1' then
           aux := aux + (2**i);
19         end if;
       end loop;
21     return aux;
   end vector_to_natural;

23     function natural_to_vector (nat : in natural; length : in natural)
25       return std_logic_vector is
       variable v: std_logic_vector(length-1 downto 0);
27     variable quotient, aux, i, remainder: natural;
   begin
29     aux:= nat;
       i:=0;
31     while (aux/=0) and (i<length) loop
       quotient := aux/2;
```



```

33     remainder := aux mod 2;
34     if remainder=0 then v(i):='0'; else v(i):='1';
35     end if;
36     i := i+1;
37     aux := quotient;
38   end loop;
39   for j in i to length-1 loop
40     v(j):='0';
41   end loop;
42   return v;
43 end natural_to_vector;

44
45 procedure vector_add (v1, v2 : in std_logic_vector; vo : out std_logic_vector) is
46   variable sum,long: natural;
47   begin
48     long:=v1'length;
49     sum:= vector_to_natural(v1) + vector_to_natural(v2);
50     v_result := natural_to_vector(sum,long);
51   end vector_add;
52 end arith_operations;

53
54 library IEEE;
55 use IEEE.std_logic_1164.all;
56 use work.arith_operations.all; -- The packet must be included in order to use it
57
58 entity sum is
59   port (v1,v2: in std_logic_vector; v_result : out std_logic_vector);
60 end sum;
61
62 architecture beh of sum is begin
63   p1: process(v1, v2)
64     variable sum_var: natural;
65   begin
66     vector_addu(v1, v2, sum);
67     v_result<= sum_var;
68   end process p1;
69 end beh;

```


Chapter 8

Design of a RAM Memory

By reusing all the concepts that have been described throughout this document, we can now design a kind of memory that is very common in digital circuits design and computer architecture: a RAM memory with synchronous write and asynchronous read:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  -- RAM memory with 32 8-bit words
7  entity ram is
8      port (addr: in std_logic_vector (4 downto 0);
9            we, clk: in std_logic;
10           data_i: in std_logic_vector(7 downto 0);
11           data_o: out std_logic_vector(7 downto 0));
12  end ram;
13
14  architecture archxi of ram is
15      type ram_table is array (0 to 31) of std_logic_vector(7 downto 0);
16      signal rammemory: ram_table;
17
18  begin
19      process(we, clk, addr)
20      begin
21          if clk'event and clk='1' then
22              if we = '1' then
23                  rammemory(conv_integer(addr)) <= data_i;
24              end if;
25          end if;
26      end process;
27      data_o <= rammemory(conv_integer(addr));
28  end archxi;
```

For XilinxTM users: XilinxTM recognizes the previous code as a memory, but it not synthesizes that code using the memory blocks that typically exist in FPGAs for that purpose (Block RAMs or BRAMs). In order to achieve this, one can either directly instantiate BRAMs by means of specific primitives provided by XilinxTM, or to code a generic synchronous memory with **read** and **write** ports, as well as **enable**, **write** and **read** signals, as in the code below.

The `conv_integer` function is defined in the packet `ieee.std_logic_unsigned.all`. It converts a binary vector to an integer value. Note that, in VHDL, the access index to the vectors are integer values.

```

library ieee;
2 use ieee.std_logic_1164.all;
  use ieee.std_logic_arith.all;
4 use ieee.std_logic_unsigned.all;

6 entity SRAM is generic(w: integer := 4; -- word width
                          d: integer := 4; -- number of words
                          a: integer := 2); -- address width
8 port(Clock:      in std_logic;
10      Enable:    in std_logic;
      Read:       in std_logic;
12      Write:     in std_logic;
      Read_Addr:  in std_logic_vector(a-1 downto 0);
14      Write_Addr: in std_logic_vector(a-1 downto 0);
      Data_in:    in std_logic_vector(w-1 downto 0);
16      Data_out:   out std_logic_vector(w-1 downto 0)
18 );
end SRAM;

20 architecture behavioral of SRAM is
  -- We use an array to store the memory values
22   type ram_type is array (0 to d-1) of std_logic_vector(w-1 downto 0);
   signal tmp_ram: ram_type;
24 begin

26   -- Read
   process(Clock, Read)
28   begin
       if (Clock'event and Clock = '1') then
30         if Enable = '1' then
           if Read = '1' then
32             Data_out <= tmp_ram(conv_integer(Read_Addr));
           else
34             Data_out <= (Data_out'range => 'Z'); -- All bits of Data_out are set to 'Z'
           end if;
36         end if;
       end if;
38   end process;

40   -- Write
   process(Clock, Write)
42   begin
       if (Clock'event and Clock = '1') then
44         if Enable = '1' then
           if Write = '1' then tmp_ram(conv_integer(Write_Addr)) <= Data_in;
46         end if;
           end if;
48       end if;
     end process;
50 end behavioral;

```

Chapter 9

Appendixes

9.1 Discussion about using signals vs. variables

Signals are used to connect different components in a circuit, whereas variables are used inside `process` to compute certain values. The following example illustrates this point:

```
2  entity sig_var is
   port(d1, d2, d3: in std_logic; res1, res2: out std_logic);
end sig_var;

4
architecture behv of sig_var is
6  signal sig_s1: std_logic;
begin
8
   proc1: process(d1, d2, d3)
10     variable var_s1: std_logic;
   begin
12     var_s1 := d1 and d2;
       res1 <= var_s1 xor d3;
14   end process;

16   proc2: process(d1, d2, d3)
   begin
18     sig_s1 <= d1 and d2;
       res2 <= sig_s1 xor d3;
20   end process;
end behv;
```

One could think that both `process` should return exactly the same result, since the operations that are carried out are exactly the same.

However, this is not true. Let us take a look at the simulation in Figure 9.1.

Why is `res2` set to '1' later than `res1`? The reason is that the variable `var_s1` and the signal `res1` are updated in the same simulation step in `proc1`, whereas the signals `sig_s1` and `res2` need several simulation steps in `proc2` for the update of these two signals, respectively.

When `d1=1`, `d2=1` and `d3=0`, the process `proc1` updates `var_s1` to its new value (which is '0'), and **this new value is taken in the same simulation step** to update `res1`. Therefore, `res1` is automatically set to 1. However, in `proc2`, at this same instant of time, `sig_s1` is set to 1, but nothing

 


Figure 9.1: Simulation example showing the difference between the update of signals and variables

happens to `res2` at that simulation step. Since a change in `sig_s1` does not trigger the execution of the process `proc2` (note that `sig_s1` is not in the sensitivity list of this process), `res2` remains unchanged until a new modification of `d1`, `d2` or `d3`. The next simulation step (occurring when `d1=0`, `d2=0` and `d3=1`) does not trigger the change of `res2` either. The following one (when `d1=0`, `d2=0` and `d3=1`) does trigger the modification of `res2` from 0 to 1. The problem in this case is that this modification comes too late.

As previously hinted, looking at the code of both `proc1` and `proc2`, one would expect the behavior obtained for `proc1` in both cases. Hence, `proc2` returns a wrong simulation result. Does this mean that we should better using variables inside processes instead of signals, in order to guarantee a proper and immediate update? **NOT AT ALL**. What we should do is to double-check the sensitivity list of `proc2` and to realize that the signal `sig_s1`, which is updated in that process, is missing in that sensitivity list. If added, the simulation result of `proc2` will be exactly the same as that of `proc1`. This is closely related with what is explained in Section 9.2.

9.2 Discussion about the effect of incorrectly coding the sensitivity list in a process

For XilinxTM users: When implementing a circuit, XilinxTM does not take into account the sensitivity list of a process whatsoever. This means that, if the VHDL code is not properly written, the simulation and the final implementation results will differ. Thus, it is very important to remember that **the sensitivity list of a process MUST include all the signals that are read inside it**.

The code below and the simulation in Figure 9.2 illustrate this point:

```

1  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
   entity das is
7     port(din, sel, clk : in std_logic; dout: out std_logic);
   end das;
9
   architecture Behavioral of das is
11    signal A, B, C: std_logic;
   begin
13
       Type_C: process (clk)

```

```

15  begin
16      dout <= not C;
17  end process Type_C;

19  Type_B: process (clk)
20  begin
21      if clk 'event and clk='1' then B <= not din;
22      end if;
23  end process Type_B;

25  Type_A: process (clk)
26  begin
27      A <= not din;
28  end process Type_A;

29  C<=A when (sel='0') else B;
31
end Behavioral;

```

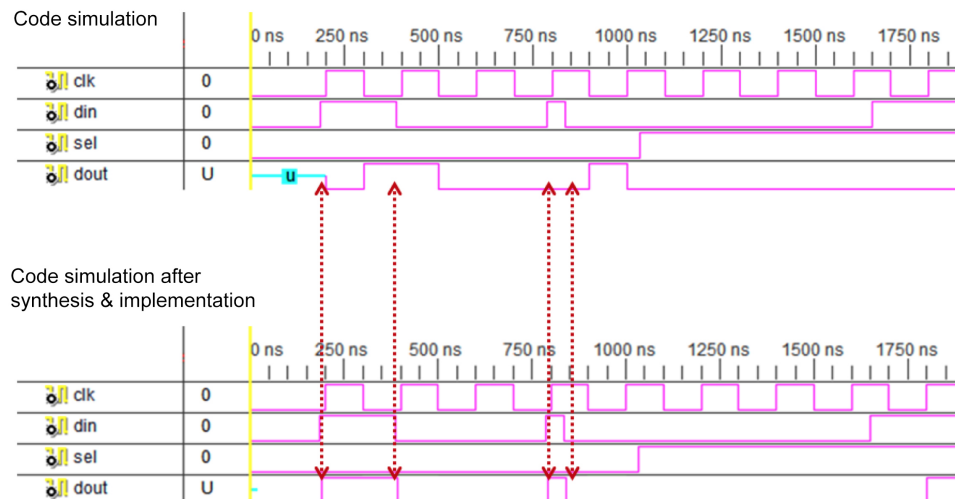


Figure 9.2: Simulation example that illustrates the effect of an incomplete sensitivity list